

$$\begin{cases} V(z) = V_{i0} e^{-rz} + V_{r0} e^{rz} \\ Z_0 \times I(z) = \frac{V_{i0}}{Z_0} e^{-rz} - \frac{V_{r0}}{Z_0} e^{rz} \end{cases}$$

$$\Rightarrow \begin{cases} V(z) = \frac{1}{2} I_L (z_L + z_0) e^{r(l-z)} + \frac{I_L}{2} (z_L - z_0) e^{-r(l-z)} \\ Z_0 \times I(z) = -\frac{I_L}{2} (z_L + z_0) e^{r(l-z)} - \frac{I_L}{2} (z_L - z_0) e^{-r(l-z)} \end{cases}$$

$$\boxed{\text{定义: } \frac{V(z)}{I(z)} = Z(z)}$$

$$\frac{Z(z)}{Z_0} = \frac{(z_L + z_0) e^{r(l-z)} + (z_L - z_0) e^{-r(l-z)}}{(z_L + z_0) e^{r(l-z)} - (z_L - z_0) e^{-r(l-z)}} \times Z_0$$

$$= \frac{z_L [e^{r(l-z)} + e^{-r(l-z)}] / 2 + z_0 [e^{r(l-z)} - e^{-r(l-z)}] / 2}{z_L [e^{r(l-z)} - e^{-r(l-z)}] / 2 + z_0 [e^{r(l-z)} + e^{-r(l-z)}] / 2} \times Z_0$$

$$= \frac{Z_L \cosh r(l-z) + Z_0 \sinh r(l-z)}{Z_L \sinh r(l-z) + Z_0 \cosh r(l-z)} \times Z_0$$

$$\boxed{Z(z) = Z_0 \frac{Z_L + Z_0 \tanh r(l-z)}{Z_0 + Z_L \tanh r(l-z)}}$$



代入 V_{i0} 和 V_{r0}
 並有 $V_L = Z_L \times I_L$

$$\Rightarrow \begin{cases} V_L = V_{i0} e^{-rl} + V_{r0} e^{rl} \\ Z_0 \times I_L = \frac{V_{i0}}{Z_0} e^{-rl} - \frac{V_{r0}}{Z_0} e^{rl} \end{cases}$$

$$\Rightarrow \begin{cases} V_{i0} = \frac{1}{2} (V_L + Z_0 I_L) e^{rl} \\ V_{r0} = \frac{1}{2} (V_L - Z_0 I_L) e^{-rl} \end{cases}$$

$$\beta = \frac{2\pi}{\lambda}$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{4} \times (2n+1)$$

$$= \frac{\pi}{2} (2n+1)$$

$$\tan \beta l \rightarrow \infty$$

$$Z_i = R_0 \frac{jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l}$$

$$Z_i = \frac{R_0^2}{Z_L}$$

$$l = \frac{\lambda}{4} \times (2n+1)$$

$$Z_i = R_0 \frac{Z_L + jR_0 \tan \beta l}{R_0 + jZ_L \tan \beta l}$$

$$l = \frac{\lambda}{2} \times n$$

$$\uparrow r = j\beta$$

$$Z_i = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}$$

$$Z_L \rightarrow \infty$$

$$Z_i = Z_0 \frac{\cancel{Z_L} + \cancel{Z_0} \tanh \gamma l}{\cancel{Z_0} + \cancel{Z_L} \tanh \gamma l}$$

$$Z_{i, \text{open}} = \frac{Z_0}{\tanh \gamma l}$$

$$\text{if lossless } r = j\beta \text{ and } Z_0 = \sqrt{\frac{L}{C}} \triangleq R_0$$

$$Z_i = \frac{R_0}{\tanh j\beta l}$$

$$Z_{i, \text{open}} = \frac{R_0}{j \tan \beta l}$$

$$\beta = \frac{2\pi}{\lambda}$$

$$\beta l = \frac{2\pi}{\lambda} \times \frac{\lambda}{2} n = \pi n$$

$$\tan \pi n = 0$$

$$Z_i = R_0 \frac{\cancel{Z_L} + j\cancel{R_0} \tan \beta l}{\cancel{R_0} + j\cancel{Z_L} \tan \beta l}$$

$$Z_i = Z_L$$

$$Z_L \rightarrow 0$$

$$Z_i = Z_0 \frac{\cancel{Z_L} + \cancel{Z_0} \tanh \gamma l}{\cancel{Z_0} + \cancel{Z_L} \tanh \gamma l}$$

$$Z_{i, \text{short}} = Z_0 \tanh \gamma l$$

if lossless

$$Z_{i, \text{short}} = jR_0 \tan \beta l$$

$$Z_{i, \text{open}} \times Z_{i, \text{short}} = Z_0^2$$

$$Z_0 = \sqrt{Z_{i, \text{open}} \times Z_{i, \text{short}}}$$

$$\sqrt{\frac{Z_{i, \text{short}}}{Z_{i, \text{open}}}} = (\tanh \gamma l)$$

$$r = \frac{1}{l} \tanh^{-1} \left[\sqrt{\frac{Z_{i, \text{short}}}{Z_{i, \text{open}}}} \right]$$

$$Z_{i_{open}} = \frac{R_o}{j \tan \beta l}$$

$$\downarrow l \ll \lambda$$

$$\beta l = \frac{2\pi}{\lambda} l$$

$$\text{if } l \ll \lambda$$

$$\text{then } \beta l \ll 1$$

$$\tan \beta l \cong \beta l$$

$$\beta = \frac{2\pi}{\lambda}$$

$$\omega = \frac{2\pi}{T}$$

$$\frac{\omega}{\beta} = V_p = \frac{1}{\sqrt{LC}}$$

$$\beta = \omega \sqrt{LC}$$

$$Z_{i_{open}} \cong \frac{R_o}{j \beta l}$$

$$= \frac{\sqrt{\frac{L}{C}}}{j \omega \sqrt{LC} l}$$

$$= \frac{1}{j \omega C l}$$

$$Z_{i_{short}} = j R_o \tan \beta l$$

$$\downarrow l \ll \lambda$$

$$Z_{i_{short}} = j R_o \beta l$$

$$= j \sqrt{\frac{L}{C}} \times \omega \sqrt{LC} l$$

$$= j \omega L l$$